

# EEE 5320

## Cadence Assignment

### 3 Format: Report

#### Objectives:

1. Getting familiar with simulation in Cadence
2. Getting familiar with different current mirror structures

#### Part A. Basic Current Mirror

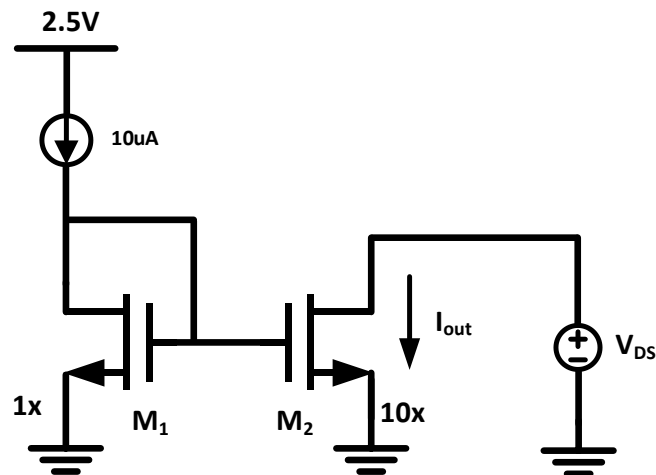


Figure 1. Basic Current Mirror

- 1) Build the circuit in Cadence as shown in Figure 1. Assume  $1x = 0.5\mu/0.18\mu$  and  $V_{DS} = 1.5V$ . What is the value of  $I_{out}$ ? Use screenshot of DC simulation to prove your result.
- 2) If  $V_{DS} = 1V$  and  $2V$ , what will be the value of  $I_{out}$  under these two cases? Use screenshot of DC simulation to prove your result.
- 3) If  $1x = 1\mu/1\mu$  and  $V_{DS} = 1.5V$ . What is the value of  $I_{out}$ ? Use screenshot of DC simulation to prove your result.
- 4) If  $1x = 1\mu/1\mu$  and  $V_{DS} = 1V$  and  $2V$ , what will be the value of  $I_{out}$  under these two cases? Use screenshot of DC simulation to prove your result.
- 5) Compare the results from 2) and 4). What is the difference and what can be the cause of that?

## Part B. Cascode Current Mirror

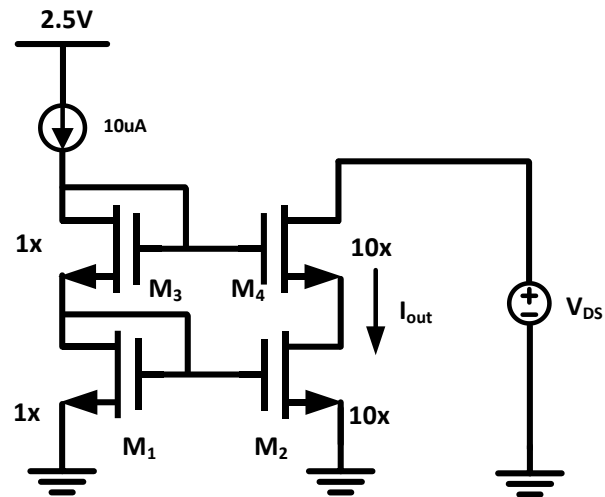


Figure 2. Cascode Current Mirror

- 1) Build the current mirror as shown in Figure 2. Repeat question 1) to 4) from Part A.
- 2) Compare with the results from 2) & 4) in Part A. What is the benefit of this cascode current mirror and what can be the cause?

## Part C. Wide-Swing Current Mirror

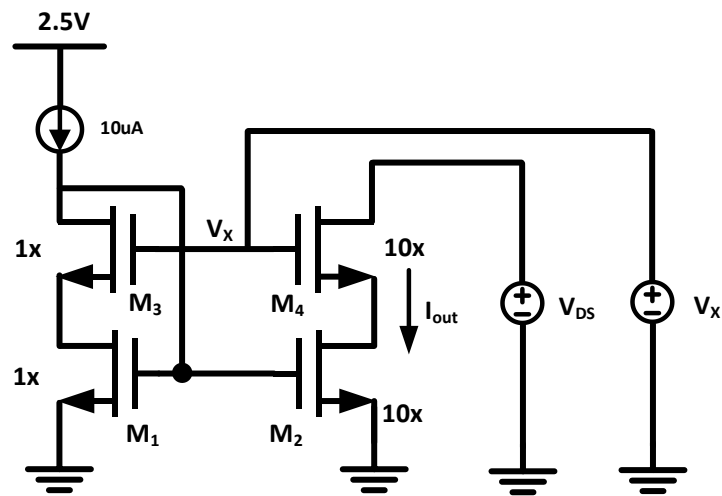


Figure 3. Wide-swing Current Mirror

- 1) Build the current mirror as shown in Figure 3. Assume  $1x = 1\mu/1\mu$ ,  $V_{DS} = 1.5V$  and  $V_X = 1V$ . What is the value of  $I_{out}$ ? Use screenshot of DC simulation to prove your result.
- 2) If  $V_{DS} = 1V$  and  $2V$ , what will be the value of  $I_{out}$  under these two cases? Use screenshot of DC simulation to prove your result.
- 3) What is the minimum  $V_X$  that can set all transistors in saturation? Compare with  $V_X = 1V$ , how does the  $I_{out}$  change with different  $V_{DS}$ ?
- 4) Compare with the results from 1) in Part B. What is the difference? What is the biggest advantage of this wide-swing structure?